

RLC 电路的谐振现象

2300011403 杨轶

November 2023

1 测量谐振频率与第一种 Q 值

通过李萨如图形，可得出

$$f_0 = 2.2495 \text{ kHz}, \Delta f_0 = 0.0001 \text{ kHz}$$

实验器材参数：标准电阻 $R = 100.00\Omega$, $\Delta R = 0.01\Omega$ ；电容箱 $C = 0.05 \mu\text{F}$ ，允差约 0.65%；电感 $L = 0.1 \text{ H}$ ，允差约 0.1%，内阻 $R_L = 18.033\Omega$ 。

$$Q_1 = \frac{2\pi f_0 L}{R + R_L} = 11.975 \quad (1)$$

$$\sigma_{f_0} = \frac{\Delta f_0}{\sqrt{3}}, \sigma_L = \frac{0.1\% L}{\sqrt{3}}, \sigma_R = \frac{\Delta R}{\sqrt{3}}$$

$$\sigma_{Q_1} = Q_1 \sqrt{\left(\frac{\sigma_{f_0}}{f_0}\right)^2 + \left(\frac{\sigma_L}{L}\right)^2 + \left(\frac{\sigma_R}{R + R_L}\right)^2} = 0.007 \quad (2)$$

$$Q_1 = 11.975 \pm 0.007 \quad (3)$$

2 第二种 Q 值

$$U_{in} = 1.0234 \text{ V}$$

$$U_L = 10.745 \text{ V}$$

$$U_C = 10.715 \text{ V}$$

$$Q_2 = \frac{U_C}{U_{in}} = 10.470 \quad (4)$$

数字多用表交流档允差约为 0.2% + 10 个字

$$\Delta U_{in} = 0.2\% U_{in} + 0.0010 = 0.003, \sigma_{U_{in}} = \frac{\Delta U_{in}}{\sqrt{3}}$$

$$\Delta U_C = 0.2\%U_C + 0.010 = 0.04, \sigma_{U_C} = \frac{\Delta U_C}{\sqrt{3}}$$

$$\sigma_{Q_2} = Q_2 \sqrt{\left(\frac{\sigma_{U_C}}{U_C}\right)^2 + \left(\frac{\sigma_{U_{in}}}{U_{in}}\right)^2} = 0.05 \quad (5)$$

$$Q_2 = 10.47 \pm 0.05 \quad (6)$$

经对比发现， Q_1 与 Q_2 相差远大于其误差，将通过后面 Q_3 的计算来判断是否合理。

3 相频特性

相差 $\phi = f_i \Delta t$

i	1	2	3	4	5	6	7	8
f_i/kHz	1.000	1.200	1.600	1.800	2.000	2.100	2.200	2.300
$\Delta t/\mu\text{s}$	-0.246ms	-0.202ms	-144.5	-120.0	-95.0	-73.0	-32.0	30.5
$\phi/^\circ$	-88.56	-87.26	-83.23	-77.76	-68.40	-55.19	-25.34	25.254

i	9	10	11	12	13
f_i/kHz	2.500	2.700	2.900	3.200	3.600
$\Delta t/\mu\text{s}$	71.0	75.0	74.5	72.0	65.5
$\phi/^\circ$	63.90	72.90	77.79	82.94	84.89

表 1: 电路相频特性数据表

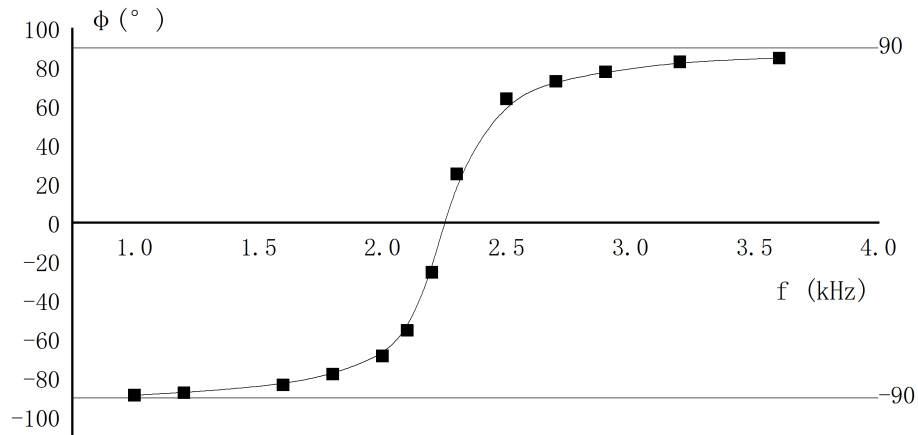


图 1: 相频曲线

4 幅频特性

固定输入电压 $U_{in} = 1V$

电流 $I = \frac{U_R}{R}$

i	1	2	3	4	5	6	7	8
f_i/kHz	1.000	1.200	1.500	1.800	1.900	2.000	2.100	2.150
U_R/mV	39.21	52.68	84.43	153.84	200.52	279.21	0.4257V	0.5442V
I/mA	0.3921	0.5268	0.8443	1.5384	2.0052	2.7921	4.257	5.442
i	9	10	11	12	13	14	15	16
f_i/kHz	2.200	2.220	2.240	2.250	2.260	2.280	2.300	2.350
U_R/V	0.6837	0.7283	0.7534	0.7564	0.7524	0.7264	0.6826	0.5518
I/mA	6.837	7.283	7.534	7.564	7.524	7.264	6.826	5.518
i	17	18	19	20	21	22	23	
f_i/mV	2.400	2.500	2.600	2.800	3.000	3.200	3.600	
U_R/mV	0.4420V	305.38	231.35	156.58	119.43	97.31	72.04	
I/mA	4.420	3.0538	2.3135	1.5658	1.1943	0.9731	0.7204	

表 2: 电路幅频特性数据表

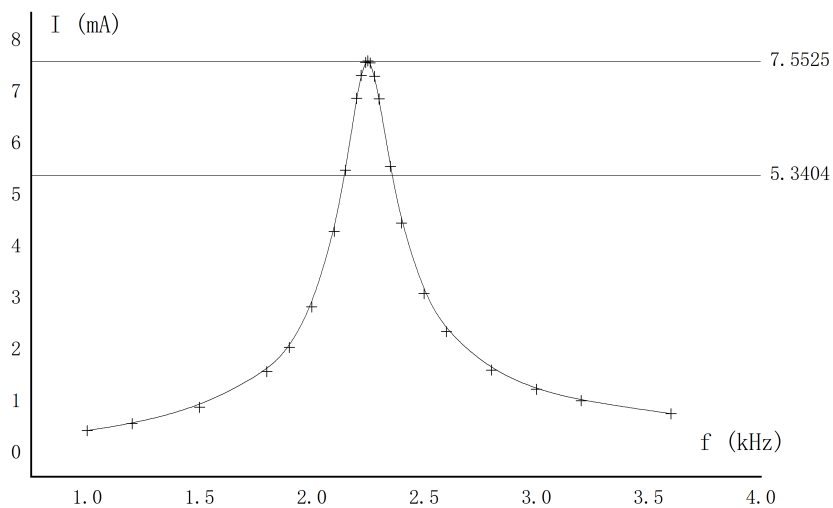


图 2: 幅频曲线

峰值坐标: $f_0 = 2.2494 \text{ kHz}$, $I_m = 7.5525 \text{ mA}$

$$\frac{I_m}{\sqrt{2}} = 5.3403 \text{ kHz}$$

f_1 与 f_2 对应电流为 $I_m/\sqrt{2}$

$$f_1 = 2.1446 \text{ kHz}, f_2 = 2.3590 \text{ kHz}$$

$$\Delta f = f_2 - f_1 = 0.2144 \text{ kHz}; \quad (7)$$

$$Q_3 = \frac{f_0}{\Delta f} = 10.492 \quad (8)$$

5 关于 Q 值的讨论

我们发现 Q_2 与 Q_3 相差并不大, 但 Q_1 与 Q_2, Q_3 有明显的差异。我们认为这是由于电路中存在由交流造成的阻抗所导致的。我们可以算出在谐振条件下回路总电阻 R' 。

$$\frac{R'}{R} = \frac{U_{in}}{U_R} \quad (9)$$

$$U_{in} = 1.0232 \text{ V}, U_R = 0.7673 \text{ V}$$

$$R' = \frac{U_{in}}{U_R} R = 133.4 \Omega \quad (10)$$

姓名 杨帆 学号 2300011403

星期 第 组

页码 1 /

1. 谐振频率 f_0 与 Q_1

$$R = 100.00 \pm 0.01 \Omega \quad L = 0.1 \text{ H} \quad R_L = 18.033 \Omega$$

李希如图 $f_0 = 2.2495 \text{ kHz}$

$$\Delta f_0 = 0.0001 \text{ kHz}$$

$$C = 0.05 \mu\text{F}$$

$$\sigma_{f_0} = \frac{\Delta f_0}{f_0}$$

$$Q_1 = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R} = 14.134$$

$$\Delta L = 0.1\% \cdot L \quad \sigma_L = \frac{\Delta L}{L}$$

$$\sigma_R = \frac{\Delta R}{R}$$

$$\sigma_{Q_1} = Q_1 \cdot \sqrt{\left(\frac{\sigma_{f_0}}{f_0}\right)^2 + \left(\frac{\sigma_L}{L}\right)^2 + \left(\frac{\sigma_R}{R}\right)^2} = 0.009$$

$$\Delta C = 0.65\% \cdot C$$

$$\sigma_C = \frac{\Delta C}{C}$$

$$2. \quad Q_2 = \frac{U_L}{U_{in}} = \frac{U_C}{U_{in}}$$

$$Q_1 = \frac{1}{R \omega_0 C} = \frac{1}{2\pi f_0 R C} = 14.150$$

$$Q_1 = \frac{\omega_0 L}{R + R_L} = 11.975$$

$$\sigma_{Q_2} = Q_2 \cdot \sqrt{\left(\frac{\sigma_R}{R}\right)^2 + \left(\frac{\sigma_{f_0}}{f_0}\right)^2 + \left(\frac{\sigma_C}{C}\right)^2} = 0.06$$

$$2. \quad Q_2 = \frac{U_L}{U_{in}} = \frac{U_C}{U_{in}}$$

$$U_{in} = 1.0281 \text{ V}$$

$$U_L = 10.625 \text{ V}$$

$$U_C = 10.598 \text{ V} \quad \checkmark$$

$$\begin{array}{l} 34 \\ 1.0281 \text{ V} \\ 45 \\ 10.715 \text{ V} \\ 10.691 \text{ V} \\ 10.715 \end{array}$$

$$Q_2 = \frac{U_L}{U_{in}} = 10.334$$

$$Q_2 = \frac{U_C}{U_{in}} = 10.308 \quad \checkmark$$

$$10.470$$

3. 相频特性

i	1	2	3	4	5	6	7
f_i / kHz	1.000	1.200	1.400	1.600	1.800	2.000	2.100
$\Delta t / \text{ms}$	-0.24	-0.202	-0.168	-144.5 μs	-120.0 μs	-95.0 μs	-73.0 μs
T / ms	1.000						

i	8	9	10	11	12	13	14
f_i / kHz	2.200	2.300	2.500	2.700	2.900	3.200	3.600
$\Delta t / \mu\text{s}$	-32.0	30.5	71.0	75.0	74.5	72.0	65.5

图 3: 课上报告

姓名 杨帆

学号 2300011403

星期 第 组

页码 2 /

4. 幅频特性

 $U_{in} = 1V$

i	1	2	3	4	5	6	7
f/kHz	1.000	1.200	1.500	1.800	1.800 1.900	1.950	2.000
U_R/mV	39.21	52.68	84.43	153.84	200.52	224.73	260.16 279.21
i	8	9	10	11	12	13	14
f/kHz	2.050	2.100	2.150	2.200	2.250 2.250	2.240	2.250
U_R/mV	319.30	0.4257V 0.3874V	0.5442V 0.4774V	0.6837V 0.5748V	0.7283V	0.7534V	0.7564V
i	15	16	17	18	19	20	21
f/kHz	2.260	2.280	2.300	2.350	2.400	2.500	2.500
U_R/mV	0.7524V	0.7264V	0.6826V	0.5518V	0.4420V	305.38mV	231.35
i	22	23	24	25			
f/kHz	2.800	3.000	3.200	3.500			
U_R/mV	156.58	119.43	97.41	72.04			

同路中总电阻 R'

$$\frac{R'}{R} = \frac{U_{in}}{U_R}$$

$$U_{in} = \frac{1.0232}{10.232} V$$

$$U_R = 0.7673V$$

$$\Rightarrow R' = 133.4 \Omega$$